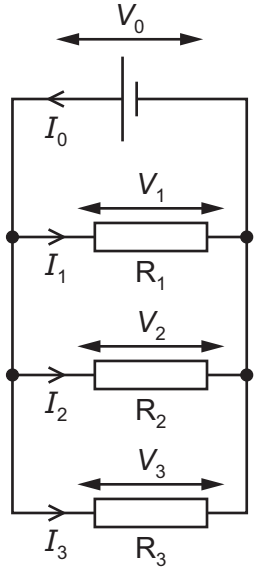
35 Three resistors, R_1, R_2 and R_3, are connected in parallel to a cell. The currents in the resistors are I_1, I_2 and I_3. The potential differences across the resistors are V_1, V_2 and V_3. The current in the cell is I_0. The potential difference across the cell is V_0, as shown.



Which equation can be obtained by applying Kirchhoff's second law to the circuit?

A $I_0 = I_1 = I_2 = I_3$

B $I_0 = I_1 + I_2 + I_3$

C $V_0 = V_1 = V_2 = V_3$

D $V_0 = V_1 + V_2 + V_3$