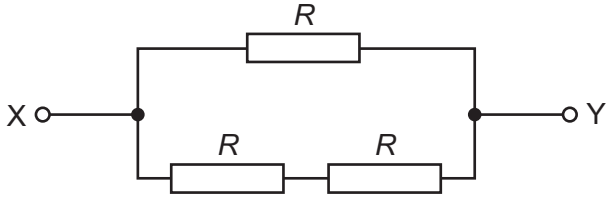
36 Three resistors, each of resistance R, are connected in a network, as shown.



The total resistance between points X and Y is 8.0 Ω.

What is the value of R?

A 2.7 Ω **B** 4.0 Ω **C** 5.3 Ω **D** 12 Ω