31 Kirchhoff's second law is a consequence of a basic principle.

What is this principle?

A The charge flowing in an electric circuit is conserved.

B The energy in an electric circuit is conserved.

C The sum of the electric currents entering a point in an electric circuit is equal to the sum of the electric currents leaving that point.

D The sum of the potential differences in an electric circuit is equal to the sum of the products of the current and resistance.