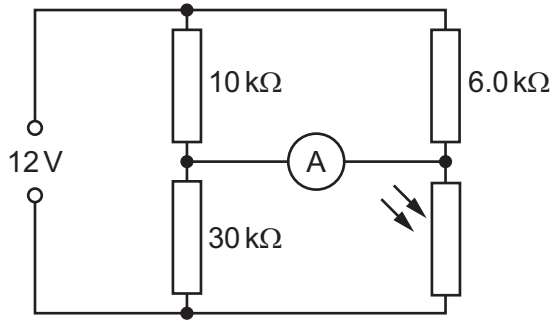
32 The diagram shows a circuit with a light-dependent resistor (LDR).



The ammeter reads zero current.

What is the resistance of the LDR?

A 6.0 kΩ **B** 18 kΩ **C** 26 kΩ **D** 30 kΩ