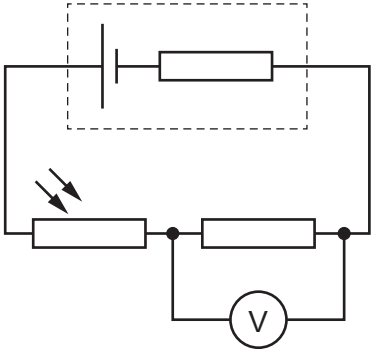
34 A cell with internal resistance is connected to a light-dependent resistor (LDR), a fixed resistor and a voltmeter, as shown.



The voltmeter reading increases.

Which quantity decreases as the voltmeter reading increases?

A the charge moving through the cell per unit time

B the energy transferred to the fixed resistor per unit charge

C the intensity of the light incident on the LDR

D the terminal potential difference across the cell