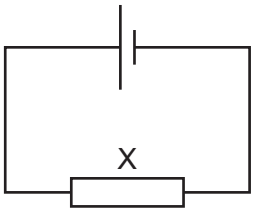
35 The circuit shown contains a cell with negligible internal resistance.



The energy transferred per unit charge in driving charge around the complete circuit is *E*. The potential difference (p.d.) across X is *V*.

The cell is then replaced with a different cell of the same electromotive force (e.m.f.) that has significant internal resistance.

What is the effect on *E* and *V* of replacing the cell?

	effect on *E*	effect on *V*
A	decreases	decreases
B	decreases	increases
C	no change	decreases
D	no change	increases