

35 Three resistors are connected to a cell of negligible internal resistance.

Which circuit has a combined resistance of 100 Ω?


A

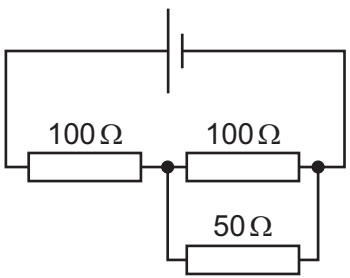

B

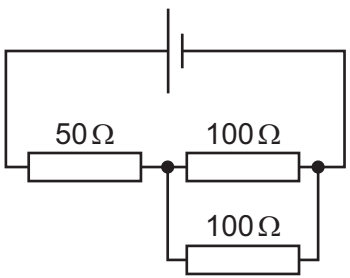

C

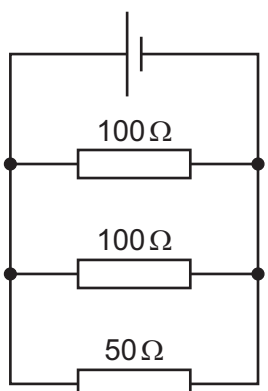

D

