37 A cell with electromotive force (e.m.f.) 1.50 V delivers a current of 0.26 A to a resistor of resistance 5.0 Ω connected between its terminals.

What is the internal resistance of the cell?

A 0.04 Ω **B** 0.20 Ω **C** 0.39 Ω **D** 0.77 Ω