

33 A fixed resistor and a diode are combined by connecting them in series. The total potential difference V across the combination is varied and the corresponding current I is measured.

Which graph could represent the variation of I with V?


A

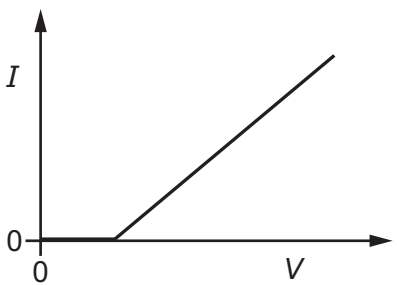

B

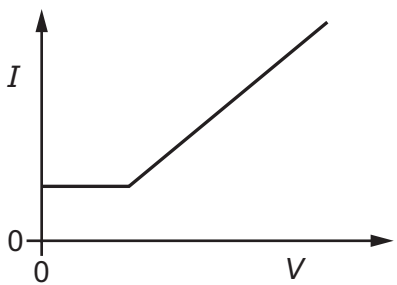

C

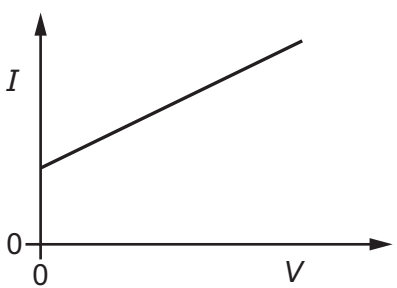

D

