
**36** The diagram shows a circuit.

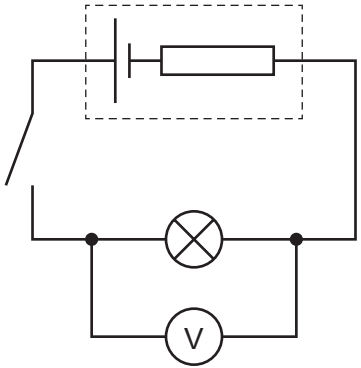


Which statement about the circuit is **not** correct?

**A** Electromotive force is the energy transferred per unit charge.

**B** Energy is transferred from chemical potential energy in the cell to other forms when the switch is closed.

**C** The electromotive force of the cell is greater than the terminal potential difference when the switch is closed.

**D** When the switch is open, the voltmeter measures the electromotive force of the cell.