28 A student connects a resistor of resistance R in parallel with a cell of electromotive force (e.m.f.) V.

Which calculation gives the current I in the resistor?

A $\frac{R}{V}$ **B** $R \times V$ **C** $\frac{V}{R}$ **D** $V + R$