29 A light-emitting diode (LED) is connected to a battery and glows.

The LED is then connected to the battery the other way round.

Which statement is correct?

A The LED will **not** glow.

B The LED will still glow but less brightly.

C The LED will glow more brightly.

D The current in the LED will be too large.

PapaCambridge
papacambridge.com