30 The diagram shows a battery connected to four resistors.

The resistances of the resistors are as labelled.

At which point in the circuit is the current the lowest?

