
31 The circuit shown can be completed by inserting components at X and at Y.

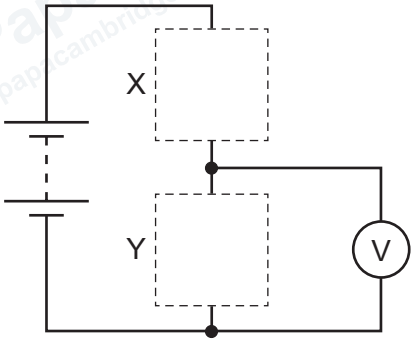The completed circuit is a potential divider in which the potential difference (p.d.) across component Y increases when the temperature increases.



Which row shows the components X and Y?

	X	Y
A	light-dependent resistor	resistor
B	resistor	light-dependent resistor
C	resistor	thermistor
D	thermistor	resistor