28 There is an electric current I in a resistor for a time t.

The potential difference (p.d.) across the resistor is V.

Which equation can be used to calculate the energy E transferred in the resistor?

A $E = I \times V \times t$ **B** $E = \frac{I \times V}{t}$ **C** $E = \frac{I}{V \times t}$ **D** $E = \frac{V}{I \times t}$