29 Two resistors, X and Y, are connected in parallel.

The two resistors have a combined resistance of 24 Ω.

Resistor X has a resistance of 40 Ω.

What is the resistance of resistor Y?

A 16 Ω **B** 32 Ω **C** 60 Ω **D** 64 Ω