33 A 100% efficient transformer has 4500 turns on its primary coil and 900 turns on its secondary coil.

The primary coil is supplied with a current of 1.5 A at a voltage of 240 V.

What is the current in the secondary coil?

A 0.30 A **B** 7.5 A **C** 160 A **D** 360 A