28 A teacher makes four circuits with two identical lamps, J and K.

In which circuit will **only** lamp J light?

