

29 Which combination has a resistance of 8.0 Ω?


A

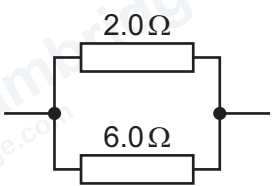

B

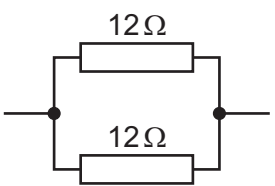

C

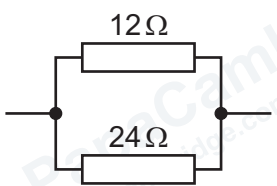

D

