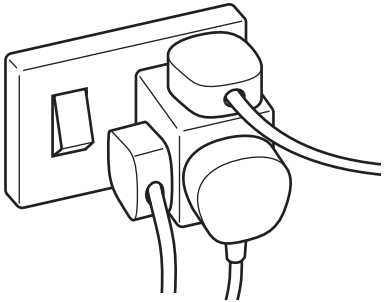
30 Multiple sockets can be connected to the mains electricity supply so that a lot of appliances can use the same socket.



Why can this be a problem?

A The current in each appliance may **not** be enough for it to work correctly.

B The potential difference (p.d.) across each appliance may **not** be enough for it to work correctly.

C The total current may be large and cause overheating or a fire.

D The total potential difference (p.d.) may be large and cause overheating or a fire.