
33 A 12 V, 36 W lamp shines at normal brightness when connected to a mains transformer.

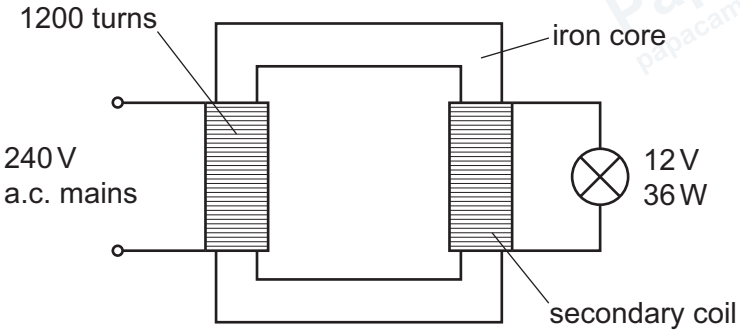Assume the transformer is 100% efficient.



Which row shows the number of turns in the secondary coil and the current in the mains wires?

	number of turns in secondary coil	current in the mains wire / A
A	60	0.15
B	60	3.0
C	180	0.15
D	180	3.0