30 Which labelled component in the circuit shown controls the brightness of lamp X?

