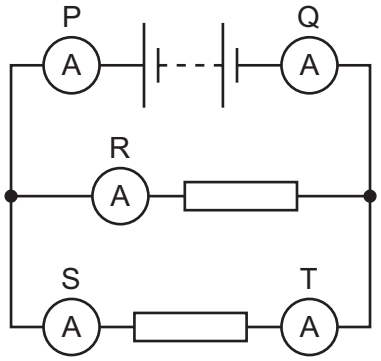
31 A circuit includes a battery, two identical resistors and five ammeters, P, Q, R, S and T.



Which statement about the readings on the ammeters is **not** correct?

A P has a greater reading than Q.

B P has a greater reading than R.

C P has a greater reading than S.

D P has a greater reading than T.