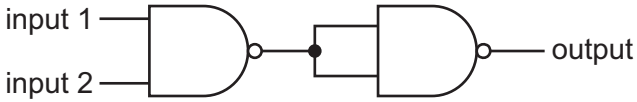
33 Two NAND gates are joined together as shown.



Which single logic gate is equivalent to this combination?

A AND **B** NAND **C** NOR **D** OR