**31** A resistor converts 360 J of energy when there is a current of 3.0 A in it. The potential difference across the resistor is 6.0 V.

For how long is there this current in the resistor?

**A** 0.05 s **B** 20 s **C** 180 s **D** 720 s