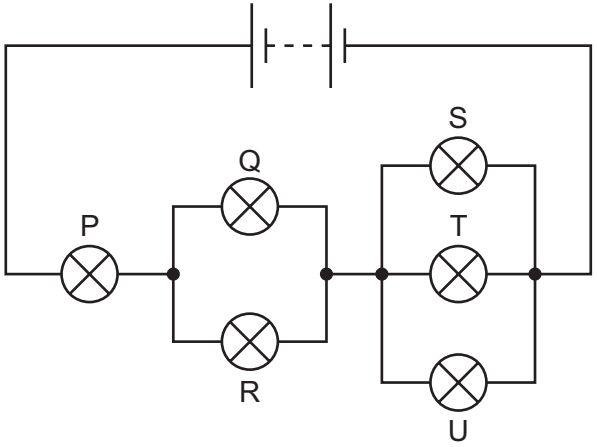
33 The diagram shows a circuit of six identical lamps connected to a battery.



Which lamps are brightest?

A P only

B Q and R only

C S, T and U only

D P, Q, R, S, T and U are equally bright