

36 Which transformer can change a 240 V a.c. input into a 15 V a.c. output?


A

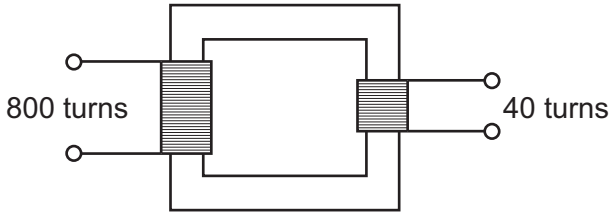

B

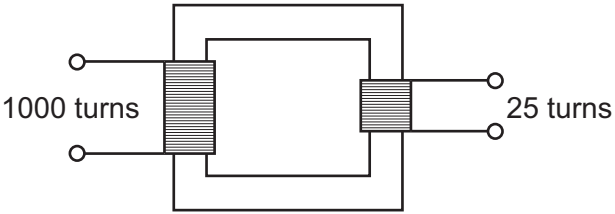

C

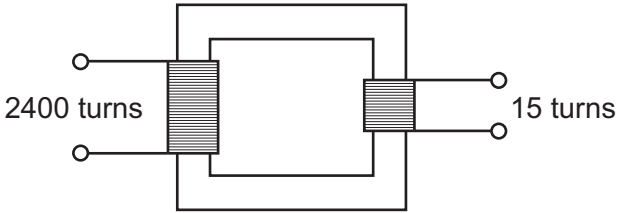

D

