30 A resistor has a potential difference (p.d.) of 12 V across it and a current of 0.60 A in it.

What is the resistance of the resistor?

A 0.050 Ω **B** 2.0 Ω **C** 7.2 Ω **D** 20 Ω