31 There is a current I in a resistor of resistance R for a time t. The potential difference (p.d.) across the resistor is V.

Which equation gives the power P dissipated in the resistor?

A $P = IR$ **B** $P = It$ **C** $P = IV$ **D** $P = \frac{IV}{t}$