26 A resistor and a battery are connected in series.

The value of the resistor is 20 Ω.

The potential difference (p.d.) of the battery is 4.0 V.

What is the current in the resistor?

A 0.20 A **B** 4.0 A **C** 5.0 A **D** 80 A