32 Which statement about identical lamps in a parallel circuit is **not** correct?

A If one lamp blows, the others remain switched on.

B The current in each lamp is different.

C The lamps can be switched on and off separately.

D The lamps have the same voltage across each of them.