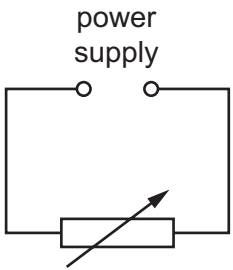
26 The diagram shows a circuit containing a variable resistor connected to a variable power supply.



The table shows the currents for different values of the potential difference (p.d.) and the resistance.

p.d. / V	resistance / Ω	current
3.6	12	I_1
1.2	12	I_2
3.6	6	I_3

What is the order of the currents from smallest to largest?

A $I_1 \rightarrow I_2 \rightarrow I_3$ **B** $I_1 \rightarrow I_3 \rightarrow I_2$ **C** $I_2 \rightarrow I_1 \rightarrow I_3$ **D** $I_3 \rightarrow I_1 \rightarrow I_2$