
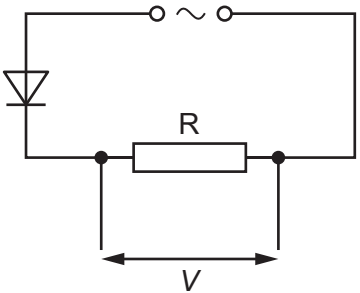
30 An alternating current (a.c.) power supply is connected in series with a resistor R and a diode.




Which graph shows how the voltage *V* across the resistor R varies with time?


A

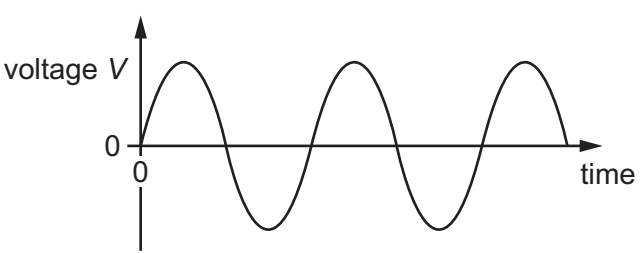

B

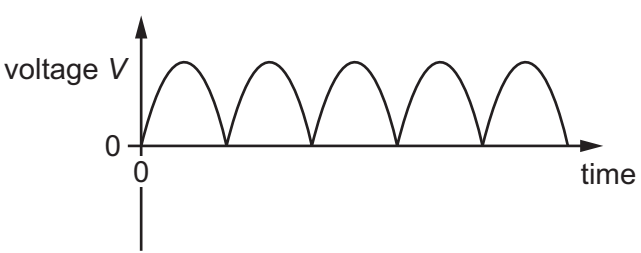

C

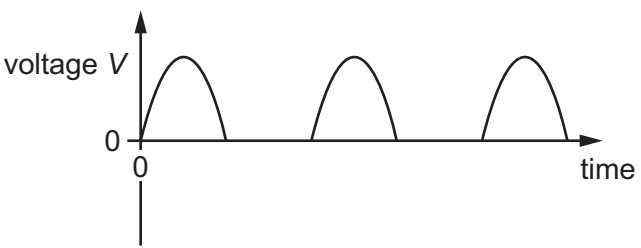

D

