

32 Which diagram shows a circuit containing a battery, a fuse and a buzzer?


A

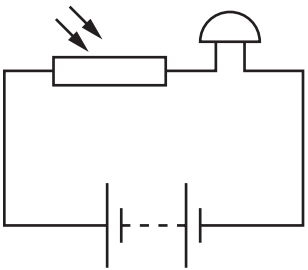

B

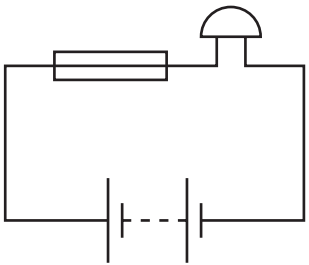

C

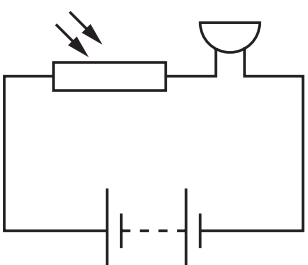

D

