
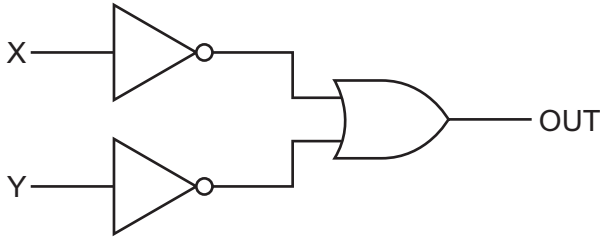
33 The diagram shows a network of logic gates.




Which single logic gate, placed between X, Y and OUT, would have the same effect as the network?


A

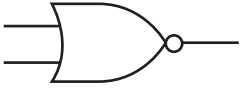

B

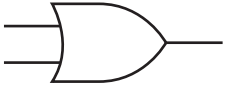

C

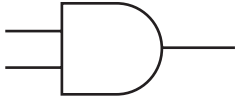

D

