
26 The diagram shows a circuit used to control the potential difference (p.d.) across a lamp.

The variable resistor is adjusted until the p.d. across the lamp is 6.0 V.

The current in the lamp is 0.5 A.

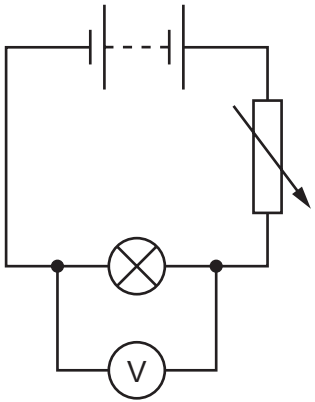

What is the resistance of the lamp?

A 0.083 Ω **B** 3.0 Ω **C** 6.5 Ω **D** 12.0 Ω