27 A charge Q flows for time t through a resistor of resistance R.

Which equation gives the current I in the resistor?

A $I = Qt$ **B** $I = Rt$ **C** $I = \frac{Q}{t}$ **D** $I = \frac{R}{t}$