31 Diagram 1 is a circuit diagram showing an a.c. power supply connected to four diodes and a resistor.

Diagram 2 shows the output voltage from the power supply.

diagram 1



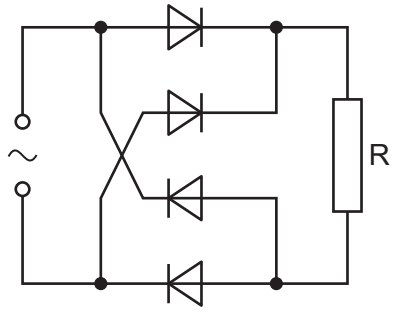


diagram 2

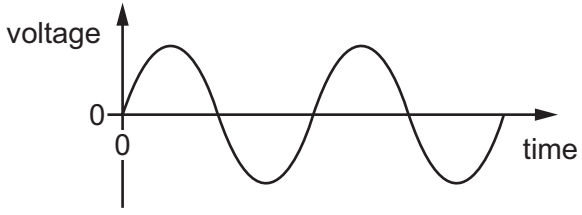


Which graph correctly shows the voltage–time curve across resistor R?


A

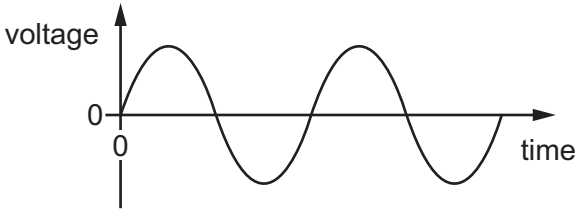

B

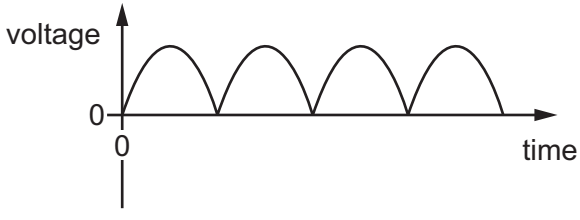

C

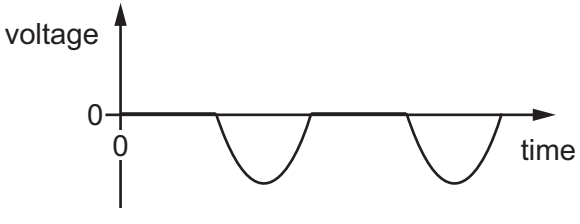

D

