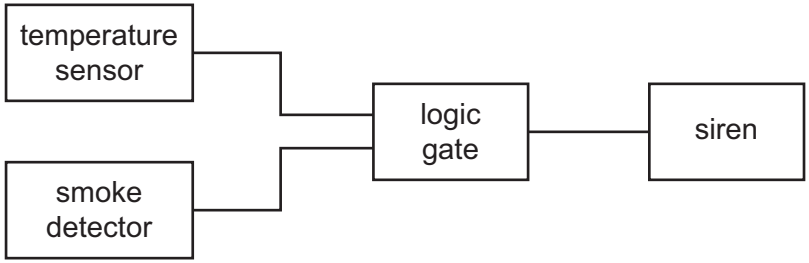
33 The diagram represents an alarm system using a logic gate.




The data for the system is shown.

state	0	1
temperature sensor	cold	hot
smoke detector	no smoke	smoke
siren	no sound	sound


The siren sounds when there is any indication of a fire.

Which logic gate is used?


A

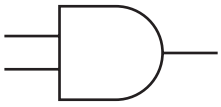

B

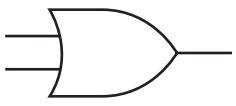

C

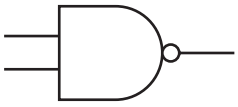

D

