
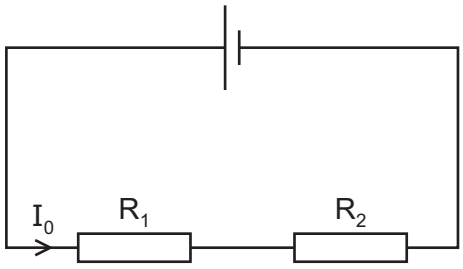
31 Two resistors, R_1 and R_2, are connected in series in a circuit, as shown.



The current in the resistors is I_0.

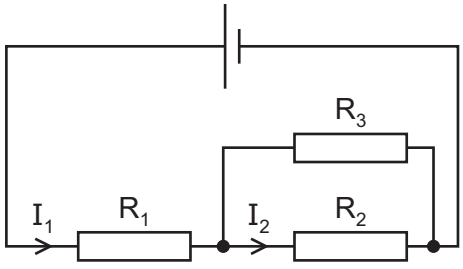Another resistor, R_3, is then connected in parallel with R_2, as shown.



How do the currents I_1 and I_2 in the resistors R_1 and R_2 compare to current I_0?

	current in R_1	current in R_2
A	$I_1 = I_0$	$I_2 < I_0$
B	$I_1 = I_0$	$I_2 = I_0$
C	$I_1 > I_0$	$I_2 = I_0$
D	$I_1 > I_0$	$I_2 < I_0$