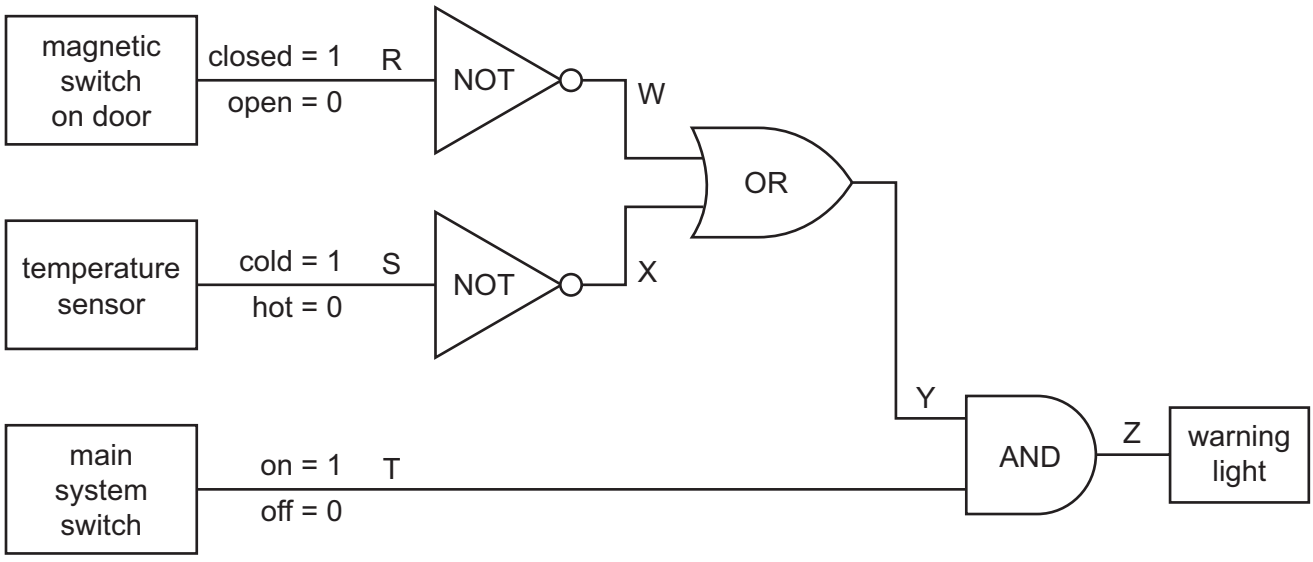
33 The diagram shows how logic gates can be used to monitor the temperature in a refrigerator.



The warning light will come on if the output at Z is 1.

The door R is open, the temperature sensor S is cold and the main system switch T is on.

What is the logic state at Y and what is the state of the warning light?

	logic state at Y	warning light
A	0	off
B	0	on
C	1	off
D	1	on